

Customized Circuit Generation

Martin Schoeberl

Technical University of Denmark

October 12, 2019

Scala List for Enumeration

```
val empty :: full :: Nil = Enum(2)
```

- ▶ Can be used in wires and registers
- ▶ Symbols for a state machine

Finite State Machine

```
val empty :: full :: Nil = Enum(2)
val stateReg = RegInit(empty)
val dataReg = RegInit(0.U(size.W))

when(stateReg === empty) {
    when(io.enq.write) {
        stateReg := full
        dataReg := io.enq.din
    }
}.elsewhen(stateReg === full) {
    when(io.deq.read) {
        stateReg := empty
    }
}
```

- ▶ A simple buffer for a bubble FIFO

Parameterization

```
class ParamChannel(n: Int) extends Bundle {
    val data = Input(UInt(n.W))
    val ready = Output(Bool())
    val valid = Input(Bool())
}

val ch32 = new ParamChannel(32)
```

- ▶ Bundles and modules can be parametrized
- ▶ Pass a parameter in the constructor

A Module with a Parameter

```
class ParamAdder(n: Int) extends Module {  
    val io = IO(new Bundle {  
        val a = Input(UInt(n.W))  
        val b = Input(UInt(n.W))  
        val result = Output(UInt(n.W))  
    })  
  
    val addVal = io.a + io.b  
    io.result := addVal  
}  
  
val add8 = Module(new ParamAdder(8))
```

- ▶ Parameter can also be a Chisel type
- ▶ Can also be a generic type:
- ▶ class Mod[T <: Bits](param: T) extends...

Scala for Loop for Circuit Generation

```
val shiftReg = RegInit(0.U(8.W))

shiftReg(0) := inVal

for (i <- 1 until 8) {
    shiftReg(i) := shiftReg(i-1)
}
```

- ▶ for is Scala
- ▶ This loop generates several connections
- ▶ The connections are parallel hardware

Conditional Circuit Generation

```
class Base extends Module { val io = new Bundle() }
class VariantA extends Base { }
class VariantB extends Base { }

val m = if (useA) Module(new VariantA())
         else Module(new VariantB())
```

- ▶ if and else is Scala
- ▶ if is an expression that returns a value
 - ▶ Like “cond ? a : b;” in C and Java
- ▶ This is not a hardware multiplexer
- ▶ Decides which module to generate
- ▶ Could even read an XML file for the configuration

Combinational (Truth) Table Generation

```
val arr = new Array[Bits](length)
for (i <- 0 until length) {
    arr(i) = ...
}
val rom = Vec[Bits](arr)
```

- ▶ Generate a table in a Scala array
- ▶ Use that array as input for a Chisel Vec
- ▶ Generates a logic table at hardware construction time

Ideas for Runtime Table Generation

- ▶ Assembler in Scala/Java generates the boot ROM
- ▶ Table with a `sin` function
- ▶ Binary to BCD conversion
- ▶ Schedule table for a TDM based network-on-chip
- ▶
- ▶ More ideas?

Memory

```
val mem = Mem(Bits(width = 8), size)

// write
when(wrEna) {
    mem(wrAddr) := wrData
}

// read
val rdAddrReg = Reg(next = rdAddr)
rdData := mem(rdAddrReg)
```

- ▶ Write is synchronous
- ▶ Read can be asynchronous or synchronous
- ▶ But there are no asynchronous memories in an FPGA

Factory Methods

- ▶ Simpler component creation and use
- ▶ Usage similar to built in components, such as Mux

```
val myAdder = Adder(x, y)
```

- ▶ A little bit more work on component side
- ▶ Define an apply method on the companion object that returns the component

```
object Adder {  
    def apply(a: UInt, b: UInt) = {  
        val adder = Module(new Adder)  
        adder.io.a := a  
        adder.io.b := b  
        adder.io.result  
    }  
}
```

Links to the Examples

- ▶ Example code

<https://github.com/schoeberl/chisel-examples.git>

- ▶ Slides

<https://github.com/schoeberl/chisel-book.git>

Feedback

- ▶ Plans on using Chisel?
- ▶ What went well?
- ▶ What was not so good?
- ▶ How can this Chisel course be improved?
- ▶
- ▶ Would be happy to receive an email: masca@dtu.dk

Lab Session

- ▶ Run and explore the UART (serial port) example
 - ▶ There is a make target that builds the UART hardware
 - ▶ `make uart`
 - ▶ It shall write some text out
 - ▶ You can observe it with a terminal (e.g., gtkterm)
- ▶ Combine the UART with a blinking LED
 - ▶ Write a '0' and '1' out on blink off and on
 - ▶ Best add the LEDs to `UartMain` and `uart_top.vhdl`
- ▶ Write repeated numbers 0–9 at maximum speed